

# IITB CPU

## EE 224 Project Report

Rohan Nafde - 210070068  
Aakarsh Chaudhary - 210070002  
Anway Deshpande - 210070011  
Geetesh Kini - 210070041

27<sup>th</sup> November, 2022

### Overview of the experiment

- We were tasked with the making of a simple programmable device.
- The device has a clock as the input and a sequence of instructions to be executed
- The contents of this report include:
  1. [Technical Specifications](#)
  2. [Approach](#)
  3. [RTL View](#)

# 1 Technical Specifications

- Processing speed of upto 50MHz on FPGA
- Memory with (specify number) of addresses
- Register file with 7 registers and 1 programme counter making for a total of 8 registers.
- Finite State Machine having only 8 states to simplify logic as much as possible.
- Memory with 64 slots, each storing 16 bit values, meaning  $2^{10} = 1\text{Kb}$  approximately

# 2 Approach

1. [Pen Paper Design](#)
2. [Instructions](#)
3. [Components Description](#)
4. [States](#)
5. [Control Design](#)

## 2.1 Pen Paper Design

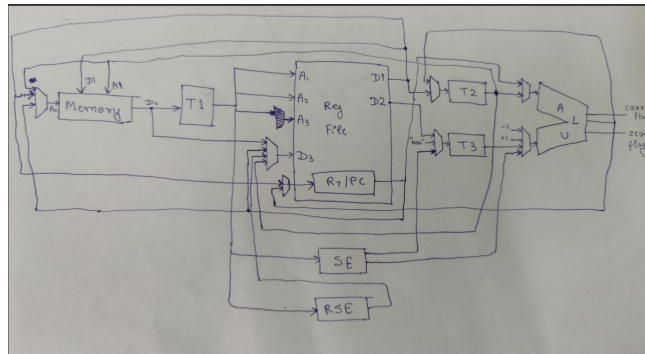


Figure 1: Pen Paper Design

## **2.2 Instructions**

### **2.2.1 Types of Instruction**

1. R Type

This type of instruction has on position(s):

- 15 to 12 - OP Code
- 11 to 9 - RA
- 8 to 6 - RB
- 5 to 3 - RC
- 2 - Unused 0
- 1 to 0 - Condition (CZ)

2. I Type

This type of instruction has on position(s):

- 15 to 12 - OP Code
- 11 to 9 - RA
- 8 to 6 - RC
- 5 to 0 - Immediate

3. J Type

This type of instruction has on position(s):

- 15 to 12 - OP Code
- 11 to 9 - RA
- 8 to 0 - Immediate

### 2.2.2 The 16 Bits of Each Instructions

Instruction	15 to 12 (OP Code)	11 to 9	8 to 6	5 to 3	2	1 to 0 (Condition CZ)
ADD	0000	RA	RB	RC	0	00
ADC	0000	RA	RB	RC	0	10
ADZ	0000	RA	RB	RC	0	01
ADI	0001	RA	RB	6 bit Immediate		
NDU	0010	RA	RB	RC	0	00
NDC	0010	RA	RB	RC	0	10
NDZ	0010	RA	RB	RC	0	01
LHI	0011	RA	9 bit Immediate			
LW	0100	RA	RB	6 bit Immediate		
SW	0101	RA	RB	6 bit Immediate		
LM	0110	RA	0 + 8 bits corresponding to Reg R7 to R0			
SM	0110	RA	0 + 8 bits corresponding to Reg R7 to R0			
BEQ	1100	RA	RB	6 bit Immediate		
JAL	1000	RA	9 bit Immediate Offset			
JLR	1001	RA	RB	000000		

Table 1: Instructions 16 bits

## **2.3 Components Description**

### **2.3.1 Arithmetic and Logic Unit**

- Two 16 bit input
- One 16 bit output, carry and zero flags too
- 2 bit control line to switch between 3 operations - ADD, SUB, NAND

### **2.3.2 Control Unit**

- Input as current state (3 bit)
- Output as 6 control lines (of write enable)
- Decides which control line should be enables

### **2.3.3 Register File**

- 3 bit input address line and 16 bit data line
- two 3 bit output address line and two 16 bit data line
- Stores the values to be immediately read or written

### **2.3.4 Memory Unit**

- 16 bit data and address line each
- Output is same too
- Stores all the

### **2.3.5 Temporary Registers**

- These just act as connections with an enabler for controlled flow

### **2.3.6 Finite State Machine**

- Initial state and inputs of CPU as input
- Next state as output
- Decides the next state

## 2.4 States

- Total 8 States
- Control decides the inputs

S1	PC $\rightarrow$ Mem_A0 Mem_D0 $\rightarrow$ T1 PC $\rightarrow$ ALU_A +1 $\rightarrow$ ALU_B ALU_C $\rightarrow$ PC	PC_WR T1_WR ADD
S2	T1 <sub>11-9</sub> /T1 <sub>8-6</sub> $\rightarrow$ RF_A1 RD_D1 $\rightarrow$ T2 T1 <sub>8-6</sub> /T1 <sub>5-0</sub> $\rightarrow$ RF_A2 RF_D2 $\rightarrow$ T3	T2_WR T3_WR
S3	T2 $\rightarrow$ ALU_A T3/+1 $\rightarrow$ ALU_B ALU_C $\rightarrow$ T2 (by op code) c=c+1	ADD/NAND
S4	(If Mem_D0 coming) T2 $\rightarrow$ Mem_A0 T1 <sub>8-0</sub> (with SE)/T2/PC/Mem_D0 $\rightarrow$ RF_D3 T1 <sub>11-9</sub> /T1 <sub>8-6</sub> /T1 <sub>5-3</sub> /c(binary) $\rightarrow$ RF_A3	RF_WR
S5	T1 <sub>11-9</sub> /c(binary) $\rightarrow$ RF_A1 RF_D1 $\rightarrow$ Mem_DI T2 $\rightarrow$ Mem_AI	Mem_WR
S6	PC $\rightarrow$ ALU_A T1 <sub>5-0</sub> /T1 <sub>8-0</sub> ALU_C $\rightarrow$ PC	PC_WR

Table 2: States

S7  $PC \rightarrow ALU\_A$  SUB  
 $+1 \rightarrow ALU\_B$   
 $ALU\_C \rightarrow PC$

S8  $T1_{8-6} \rightarrow RF\_A1$  PC\_WR  
 $RF\_D1 \rightarrow PC$

Table 3: States Continued

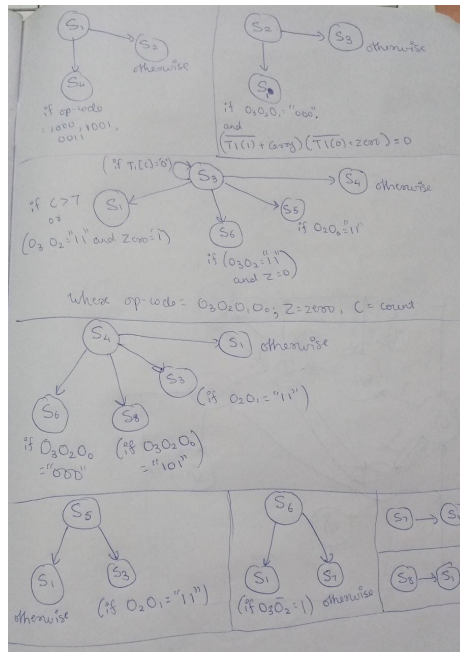


Figure 2: State transition



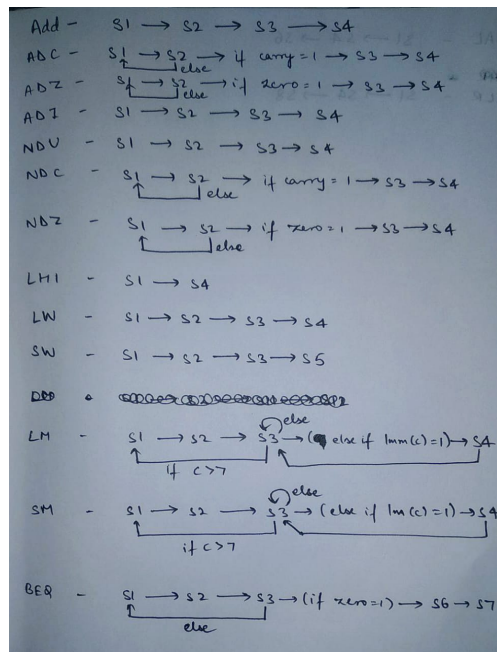


Figure 3: State Usage




 



Figure 4: State Usage Continued


## 2.5 Control Design

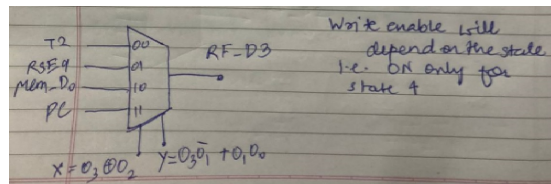

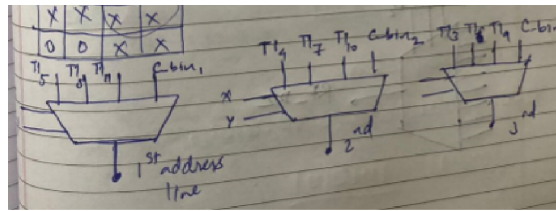



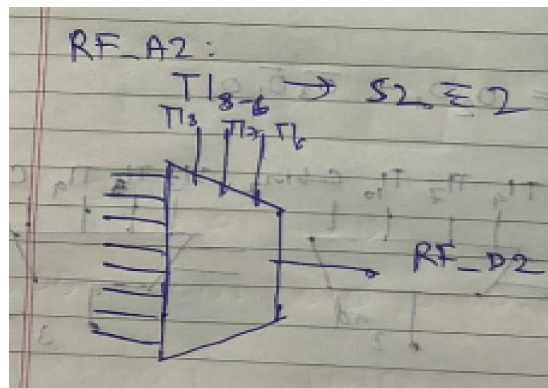


 


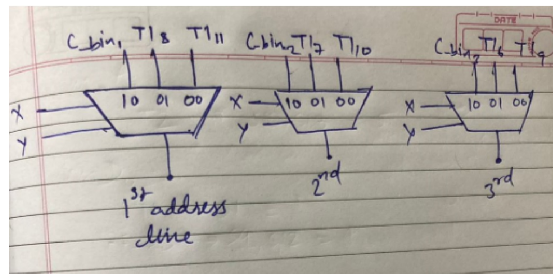


$$\begin{aligned}
 T_1-WR &= \overline{C_2} \overline{C_1} \overline{C_0} \\
 T_2-WR &= \overline{C_2} (C_1 \overline{C_0} + \overline{C_1} C_0) \\
 T_3-WR &= \overline{C_2} \overline{C_1} C_0 \\
 RF-WR &= \overline{C_2} C_1 C_0 \\
 Mem-WR &= C_2 \overline{C_1} \overline{C_0} \\
 PC-WR &= C_2 (C_1 + C_0) + \overline{C_2} \overline{C_1} \overline{C_0}
 \end{aligned}$$



---

   

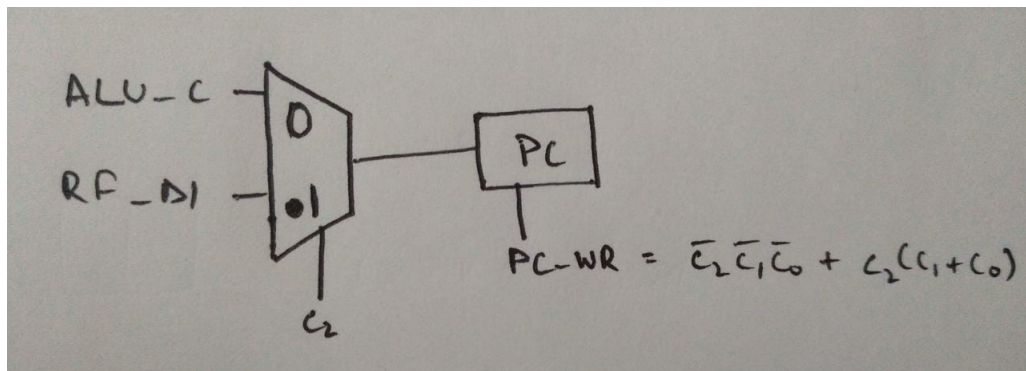



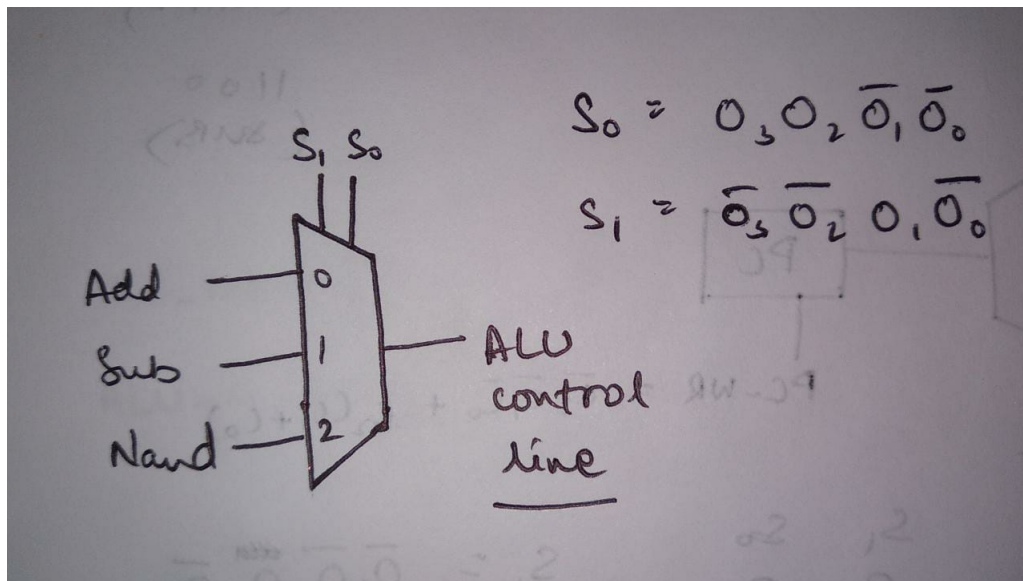 



### 3 RTL View

1. RTL View of Entire CPU

#### 3.1 RTL View of Entire CPU

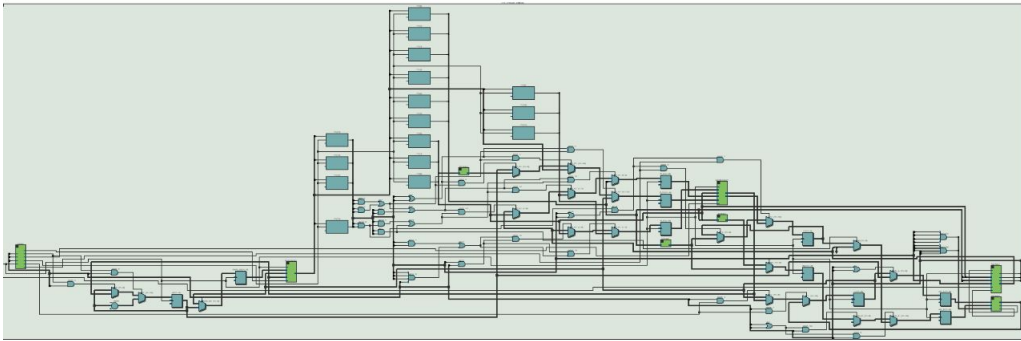


Figure 5: RTL View

## 4 Conclusion

- All the components are constructed correctly
- The components are connected correctly with the appropriate condition dependent inputs
- Instructions are correctly read
- State transitioning happens correctly
- Memory and registers are read and written correctly
- Output of all logical operations are performed correctly